
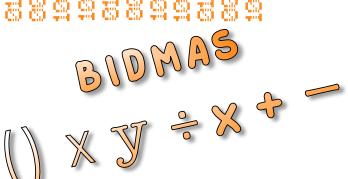
There are only 10 types of people in the world: Those who understand binary and those who don't



(AND OR B) AND (NOT C)

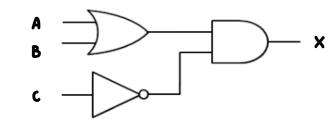



read "p implies q"



p	q	$p \Rightarrow q$
T	T	T
T	F	${f F}$
F F	T	T
F	F	T

Computer Antohmetic

The Science of Algorithms


Logic Gates & Diagrams

- Create the logic gate symbols for AND, OR, NOT
- Identify the following Boolean operations:

 $A \wedge B$ $A \vee B$ $\neg A$

What is the value at Y? Why is this?

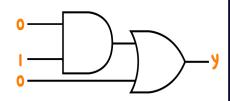- What is the alternative name for a NOT gate?
- How many input rows would you require for an AND gate?
- What would the output be for two NOT gates in series if the first input = 0



Why Binary?

- What is the link between transistors and binary?
- How many states can a binary system have?
- How many combinations could a 4 bit system have?
- What is the connection between False and 0?



Truth Tables

- Draw the truth tables for AND, OR, NOT gates
- Draw the truth table for this series of logic gates



Computer Arithmetic

What is the answer to the following:

- width = 10, length = 5 area = width * length
- gross = 100, VAT = 20, net = gross + VAT
- allHeight = 40, groupSize = 20, aveHeight = allHeight / groupSize
- salePrice = 128, commission = 10%, moneyRec = salePrice commission

- totalIncome = 75, days = 7, totalIncome **MOD** days
- ISBNnum = 132, digits = 10, ISBNnum **DIV** digits
- 2^5 =
- What is the difference between MOD and DIV?
- What is the answer to 5 + 6 / 2